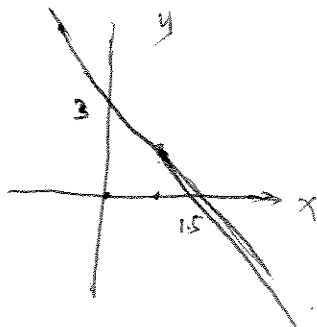


Don't waste time on problems you aren't sure of. Be clear and concise. A cluttered response will not get full credit.

1. (6 pts) Let $E_x = -2x + 3$, with E_x in volts/m and x in m. If $V = 0$ at $x = 0$, find $V(x)$. Evaluate E_x for $x = -2, -1, 0, 1, 2$ m and plot (no calculator plot; if you can't do this yourself you should ask yourself if you belong in math or science).



$$E_x = -2x + 3$$


$x = -2$	7
-1	5
0	3
1	1
2	-1

$$V(x) - V(0) = -\int_0^x (-2x + 3) dx$$

$$= +x^2 - 3x \Big|_0^x$$

$$V(x) = +x^2 - 3x$$

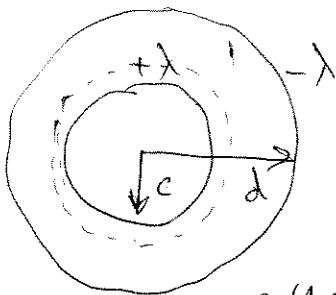2. Consider two long concentric conducting cylindrical shells of radii c and d with $c < d$. Let a charge per unit length λ be on the inner shell and $-\lambda$ be on the outer shell.



- a (4 pts) Find the electric field in the region between the plates; explain your reasoning.

$$\oint \vec{E} \cdot d\vec{A} = Q_{enc}/\epsilon_0$$

$$E \cdot 2\pi r L = \frac{\lambda L}{\epsilon_0} \Rightarrow \vec{E} = \frac{\lambda}{2\pi\epsilon_0 r} \hat{r}$$

- b (4 pts) Find $V(r) - V(d)$ for $a < r < b$.

$$V(c) - V(d) = \int_c^d \vec{E} \cdot d\vec{r} = \int_c^d \frac{\lambda}{2\pi\epsilon_0 r} \hat{r} \cdot d\vec{r} = \frac{\lambda}{2\pi\epsilon_0} \ln \frac{d}{c}$$

- c (4 pts) Find the capacitance of this system.

$$\Delta V = -(V(d) - V(c)) = \frac{\lambda}{2\pi\epsilon_0} \ln \frac{d}{c}$$


$$C = \frac{Q}{\Delta V} = \frac{\lambda L}{\frac{\lambda}{2\pi\epsilon_0} \ln \frac{d}{c}} = \frac{2\pi\epsilon_0 L}{\ln \frac{d}{c}}$$

for capacitance per unit length

$$C = \frac{C}{L} = \frac{2\pi\epsilon_0}{\ln \frac{d}{c}}$$

3. Consider three capacitors. $C_1 = 10 \mu\text{F}$ and $C_2 = 20 \mu\text{F}$ are in parallel, and $C_3 = 15 \mu\text{F}$ is in series with them. $V_A = 6 \text{ V}$ and $V_C = -4 \text{ V}$.

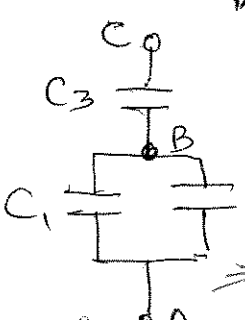a. (2 pts) Find the charge and voltage difference for each capacitor. Find V_B .



$V_A - V_C = 6 - (-4) = 10 \text{ V}$
 $C' = C_1 + C_2 = 30 \mu\text{F}$
 $\frac{1}{C} = \frac{1}{C'} + \frac{1}{C_3} = \frac{1}{30} + \frac{1}{15} = \frac{1}{10} \Rightarrow C = 10 \mu\text{F}$
 $\Rightarrow Q = C \Delta V = 10 \times 10 = 100 \mu\text{C}$
 $Q_3 = Q = 100 \mu\text{C}$
 $\Delta V_3 = \frac{Q_3}{C_3} = \frac{100 \mu\text{C}}{15 \mu\text{F}} = \frac{20}{3} \text{ V}$
 $V_B = V_C + \Delta V_3 = -4 + \frac{20}{3} = \frac{8}{3} = 2.67 \text{ V}$
 $\Delta V_1 = \Delta V_2 = V_A - V_B = 3.33 \text{ V}$

b. (2 pts) If, using insulating gloves, C_3 is disconnected and then placed in parallel with C_1 and C_2 , find the new charge and voltage difference for each capacitor.

$Q = Q_1 + Q_2 + Q_3 = 2Q_3 = 200 \mu\text{C}$
 $Q_3' = C_3 \Delta V_3 = 15 \mu\text{F} \times 4.44 \text{ V} = 66.6 \mu\text{C}$
 $C^* = C_1 + C_2 + C_3 = 10 + 20 + 15 = 45 \mu\text{F}$
 $\Delta V_1 = \Delta V_2 = \Delta V_3 = \Delta V = \frac{Q^*}{C^*} = \frac{200 \mu\text{C}}{45 \mu\text{F}} = \frac{40}{9} \text{ V} = 4.44 \text{ V}$
 $Q_1' = C_1 \Delta V_1 = 10 \mu\text{F} \times 4.44 \text{ V} = 44.4 \mu\text{C}$
 $Q_2' = C_2 \Delta V_2 = 20 \mu\text{F} \times 4.44 \text{ V} = 88.8 \mu\text{C}$

4. A parallel plate capacitor has electrical energy 3.6×10^{-7} ergs when connected to a 12 V battery. It is now disconnected from the battery. A slab of dielectric constant $\kappa = 5$ and nearly the same thickness as the capacitor is slid into the capacitor.

a. (2 pts) What is the voltage difference now?

$$\frac{12 \text{ V}}{5} = 2.4 \text{ V}$$

b. (2 pts) What is the electrical energy now?

$$\frac{1}{2} Q V = \frac{3.6 \times 10^{-7}}{5} = 0.72 \times 10^{-7}$$

c. (4 pts) Was the dielectric attracted, repelled, or did it feel no force when it was part way in the capacitor, and why? (No reason, no credit.)

5. You are given a voltaic cell with internal resistance of 3Ω . When shorted, it briefly produces a current of 0.15 A .

- a. (4 pts) Find its emf and the rate at which energy is initially discharged.

$$I = \frac{\mathcal{E}}{r} \Rightarrow \mathcal{E} = Ir = 0.15 \times 3 = 0.45 \text{ V}$$

$$P = I^2 r = (0.15)^2 (3) = 0.675 \text{ W}$$

- b. (4 pts) For what load resistance does this voltaic cell provide maximum power to load? Find that maximum power.

For impedance matching: $R = r = 3 \Omega$

$$I = \frac{\mathcal{E}}{r+R} = \frac{0.45}{6} = 0.075 \text{ A}$$


$$P_m = I^2 R = 0.075^2 \times 3 = 0.16875 \text{ W}$$

- c. (4 pts) A 100% efficient flashlight bulb of resistance R produces 1.2 W when used with a AA cell. If R is much larger than the cell's internal resistance, find R and the efficiency at which the battery produces useful power.

$$P = 1.2 \text{ W} = \frac{\mathcal{E}^2}{R}, \quad R = \frac{\mathcal{E}^2}{P} = \frac{(1.5)^2}{1.2} = 1.875 \Omega$$

6. A voltaic cell has internal resistance $r = 0.2 \Omega$ and open circuit voltages across the left and right electrodes of 0.4 V and 1.6 V , for a net emf of $\mathcal{E} = 2.0 \text{ V}$. It is in series with a resistor $R = 0.8 \Omega$. Let $V_a = 0.6 \text{ V}$. The connecting wires have zero resistance.

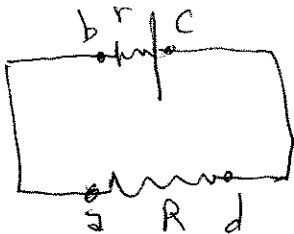
- a. (8 pts) Find the current, the voltage drops across the resistances, and sketch the voltage around the circuit.



$$I = \frac{\mathcal{E}}{r+R} = \frac{2.0}{1.0} = 2 \text{ A}$$

$$Ir = 0.4 \text{ V}$$

$$IR = 1.6 \text{ V}$$

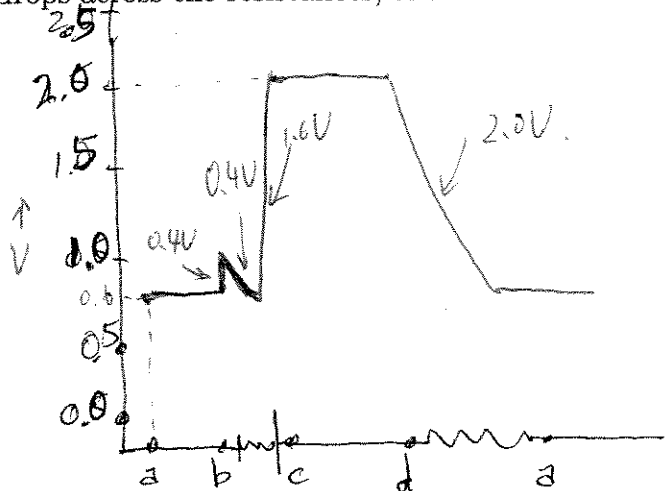

- b. (2 pts) If the voltaic cell discharges in 40 minutes, find its initial "charge" and its initial energy.

$$"Q" = It = 2 (40 \times 60) = 4800 \text{ C (or } \frac{4}{3} \text{ A-hr)}$$

$$U = \mathcal{E} "Q" = (2.0) \times (4800 \text{ C}) = 9600 \text{ J}$$

7. (6 pts) A strip of roadway has length 120 m and width 20 m. Automobiles move through it with average velocity 60 m/s, with each taking up, on average, an area of 50 m^2 . Find the rate at which the autos pass through the roadway. If they each carry a charge of $4 \times 10^{-7} \text{ C}$, find the electric current passing through the roadway.


$$\begin{aligned} \text{time to cross} &= \frac{120 \text{ m}}{60 \text{ m/sec}} = 2 \text{ sec} \\ \text{Average \# in roadway} &= \frac{120 \times 20}{50} = \frac{48}{\cancel{50}} \text{ cars} \\ \frac{dN}{dt} &= \text{rate of crossing} = \frac{48 \text{ cars}}{2 \text{ sec}} = \frac{24}{\cancel{2}} \text{ cars/sec} \\ I &= \frac{24 \text{ cars}}{\text{sec}} \times 4 \times 10^{-7} = 9.6 \times 10^{-6} \text{ A} \end{aligned}$$

8. (6 pts) Two cars, A and B, have dead batteries that are jump-started by a third car and then driven home, A going only a mile, but B going thirty miles. At home the cars are turned off and then successfully restarted. The next morning only one car will start. Which one? Why?

Car B will restart. It was given more of an average charge while being driven home.

Note! Both cars initially restarted because they were given good "surface charges", but B had more of an average charge, which leveled out over night to a large enough charge to start the car.

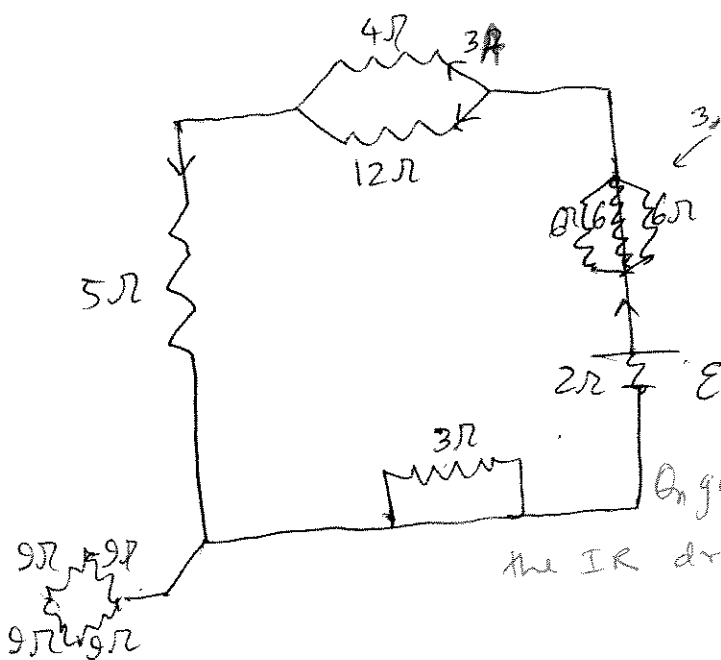9. (8 pts) Find the unknown currents, the unknown resistance, and the unknown emf for the circuit in the figure.



$$I_{12\Omega} = \frac{4\Omega \times 3\text{A}}{12\Omega} = 1\text{A}$$

$$I_{5\Omega} = 1\text{A} + 3\text{A} = 4\text{A}$$

$$I_{3\Omega} = 0 \text{ as shorted.}$$

$$I_{9\Omega} = 0 \text{ as off to the side}$$


$$I_{2\Omega} = I_{5\Omega} = 4\text{A}$$

$$I_{6\Omega} = \frac{4}{3} \text{ A [current equally divided]}$$

the IR drops sum to = $4(3) + 5(4) + 2(4) + 6(\frac{4}{3}) = 48\text{V}$

hence $E = 48\text{V}$

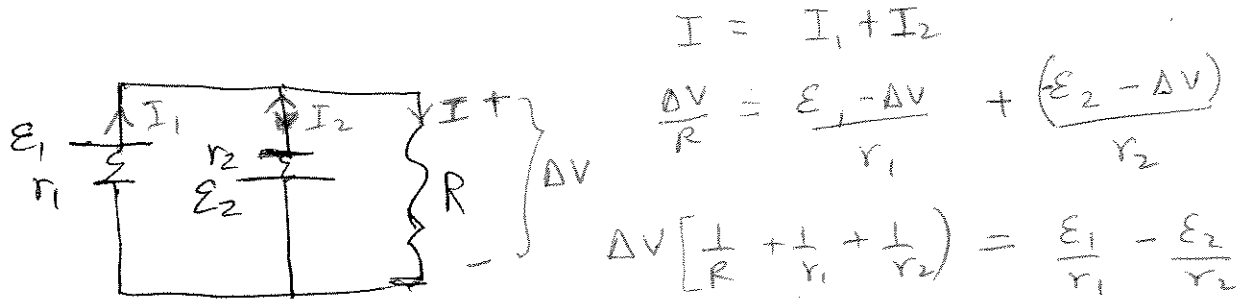10. (12 pts) For the circuit below, take $\mathcal{E}_1 = 12 \text{ V}$, $\mathcal{E}_2 = 10 \text{ V}$, $r_1 = 0.02 \Omega$, $r_2 = 0.01 \Omega$, $R = 0.03 \Omega$. (1) Indicate and label the directions of positive currents and indicate the positive side of the voltage ΔV across R . (2) Analyze the circuit using Kirchoff's rules. (3) Solve for the voltage across R . (4) Find the current through R and the currents provided by each of the batteries.



$$I = I_1 + I_2$$

$$\frac{\Delta V}{R} = \frac{\mathcal{E}_1 - \Delta V}{r_1} + \frac{(\mathcal{E}_2 - \Delta V)}{r_2}$$

$$\Delta V \left(\frac{1}{R} + \frac{1}{r_1} + \frac{1}{r_2} \right) = \frac{\mathcal{E}_1}{r_1} - \frac{\mathcal{E}_2}{r_2}$$

$$\Delta V \left(\frac{1}{0.03} + \frac{1}{0.02} + \frac{1}{0.01} \right) = \frac{12}{0.02} - \frac{10}{0.01} = 600 - 1000 = -400$$

$$\Delta V (183.3) = -400 \Rightarrow \Delta V = -2.18 \text{ V}$$


$$I = \frac{\Delta V}{R} = \frac{-2.18}{0.03} = -72.7 \text{ A}$$

$$I_1 = \frac{12 + 2.18}{0.02} = 709 \text{ A}$$

$$I_2 = -\frac{10 + 2.18}{0.01} = \frac{-7.82}{0.01} = -782 \text{ A}$$

$$I = I_1 + I_2$$

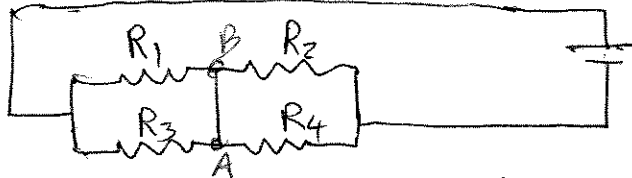11. In the circuit below the battery has an emf of 6 V.



$$R_1 = 6 \Omega, R_3 = 12 \Omega$$

$$R_2 = 24 \Omega, R_4 = 12 \Omega$$

- a. (4 pts) What is the equivalent resistance?

$$\frac{1}{R'} = \frac{1}{R_1} + \frac{1}{R_3} = \frac{1}{6} + \frac{1}{12} = \frac{3}{12} \Rightarrow R' = 4 \Omega$$

$$\frac{1}{R''} = \frac{1}{R_2} + \frac{1}{R_4} = \frac{1}{24} + \frac{1}{12} = \frac{3}{24} \Rightarrow R'' = 8 \Omega$$

$$R = R' + R'' = 4 \Omega + 8 \Omega = 12 \Omega$$

- b. (4 pts) Find the currents I_1 and I_2 , and the current from A to B, where upward current is taken to be positive.

$$I = \frac{\mathcal{E}}{R} = \frac{6}{12} = 0.5 \text{ A}$$

$$\Delta V_{123} = I R' = 0.5(4) = 2 \text{ V}$$

$$\Delta V_{24} = I R'' = 0.5(8) = 4 \text{ V}$$

$$\text{So, } I_1 = \frac{\Delta V_1}{R_1} = \frac{2}{6} = 0.33 \text{ A}$$

$$\text{So, } I_2 = \frac{\Delta V_2}{R_2} = \frac{4}{24} = \frac{1}{6} = 0.167 \text{ A}$$

A current of $(\frac{1}{3} - \frac{1}{6}) = 0.208 \text{ A}$ flows from B to A

or -0.208 A from A to B