

cgs  $\rightarrow$  1 erg =  $g\text{-cm}^2/s^2 = (10^{-3}\text{kg})(10^{-2}\text{m})^2/s^2 = 10^{-7} \frac{\text{kg}\cdot\text{m}^2}{\text{s}^2} = 10^{-7} \text{J} \leftarrow \text{MKS}$

4. A parallel plate capacitor has electrical energy  $4.8 \times 10^{-5}$  ergs when connected to a 6 V battery. It is now disconnected from the battery. A slab of dielectric constant  $\kappa = 5$  and nearly the same thickness as the capacitor is slid into the capacitor. Key Prints

- a. (3 pts) What was the initial charge on the plates?

$$U = \frac{1}{2} C (\Delta V)^2 = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} Q (\Delta V) \Rightarrow Q = \frac{2U}{\Delta V} = \frac{9.6 \times 10^{-12} \text{J}}{6\text{V}} = 1.6 \times 10^{-12} \text{C}$$

- b. (3 pts) What is the final charge on the plates?

$$Q_{\text{final}} = Q_{\text{initial}} = 1.6 \times 10^{-12} \text{C}$$

- c. (3 pts) What is the final voltage difference?

$$\Delta V_{\text{final}} = \frac{\Delta V_{\text{initial}}}{\kappa} = 1.2 \text{V}$$

- d. (3 pts) What is the final electrical energy?


$$U_{\text{final}} = \frac{1}{2} Q_{\text{in}} (\Delta V_{\text{fin}}) = \frac{1}{5} U = 0.32 \times 10^{-12} \text{J}$$

- e. (3 pts) Was the dielectric attracted, repelled, or did it feel no force when it was part way in the capacitor? No reason, no credit.

*Attracted, by the amber effect the dielectric is polarized by the charge on the plates, and then is drawn in.*


5. A voltaic cell has internal resistance  $r = 0.2 \Omega$  and open circuit voltages across the left and right electrodes of 0.3 V and 1.5 V, for a net emf of  $\mathcal{E} = 1.2 \text{V}$ . It is in series with a resistor  $R = 0.6 \Omega$ . Let  $V_b = 0.4 \text{V}$ . The connecting wires have zero resistance.

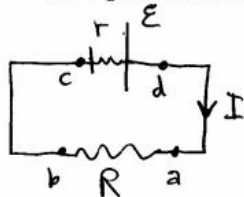- a. (10 pts) Find the current, the voltage drops across the resistances, and sketch the voltage around the circuit.



$$I = \frac{\mathcal{E}}{r+R} = \frac{1.2}{.8} = 1.5 \text{A}$$
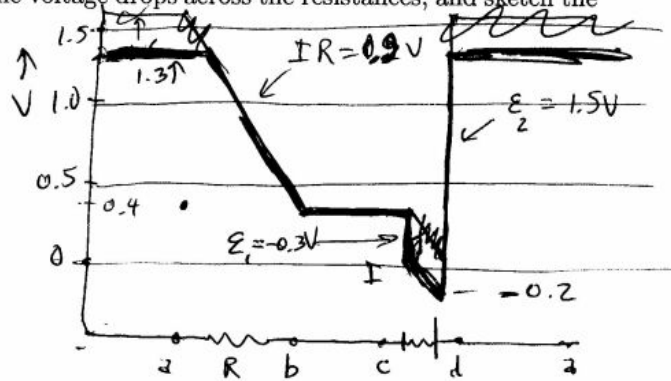
$$I r = .3 \text{V}, I R = 0.9 \text{V}$$



- b. (5 pts) If the voltaic cell discharges in 40 minutes, find its initial "charge" and its initial energy.

$$Q_0 = I T = (1.5 \text{A})(40 \times 60 \text{s}) = 3600 \text{C}$$

$$U_0 = \mathcal{E} Q_0 = (1.2)(3600) = 4320 \text{J}$$