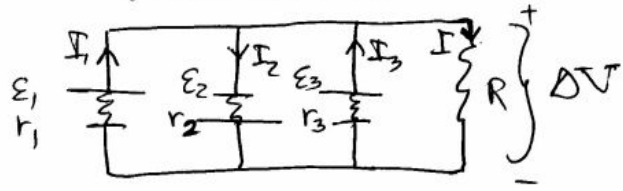


Key Points

6. (20 pts) For the circuit below, take $\mathcal{E}_1 = 6\text{ V}$, $\mathcal{E}_2 = 10\text{ V}$, $\mathcal{E}_3 = 12\text{ V}$, $r_1 = 0.02\ \Omega$, $r_2 = 0.01\ \Omega$, $r_3 = 0.03\ \Omega$, $R = 0.04\ \Omega$. Analyze the circuit using Kirchoff's rules. Solve for the voltage across R . Find the current through R and the currents provided by each of the batteries.



① Draw sign conventions ^{and definitions} for currents and voltage across R .

② Current conservation gives $I_1 + I_3 = I_2 + I$

③ $I_1 = \frac{\mathcal{E}_1 - \Delta V}{r_1}$, $I_2 = \frac{\mathcal{E}_2 + \Delta V}{r_2}$, $I_3 = \frac{\mathcal{E}_3 - \Delta V}{r_3}$, $I = \frac{\Delta V}{R}$

④ $\frac{\mathcal{E}_1 - \Delta V}{r_1} + \frac{\mathcal{E}_3 - \Delta V}{r_3} = \frac{\mathcal{E}_2 + \Delta V}{r_2} + \frac{\Delta V}{R}$, by combining ② & ③


Thus $\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_3}{r_3} - \frac{\mathcal{E}_2}{r_2} = \Delta V \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \frac{1}{R} \right)$

or $300 + 400 - 1000 = \Delta V (50 + 100 + 33.3 + 25)$, so $\Delta V = -\frac{300}{208.3} = -1.440\text{ V}$

[Thus \mathcal{E}_2 , with its low r_2 , wins as a charge pump, relative to \mathcal{E}_1 and \mathcal{E}_3 .]

⑤ $I_1 = \frac{\mathcal{E}_1 - \Delta V}{r_1} = 372.0\text{ A}$, $I_2 = \frac{\mathcal{E}_2 + \Delta V}{r_2} = 856\text{ A}$, $I_3 = 820\text{ A}$, $I = \frac{\Delta V}{R} = -36\text{ A}$, $I_2 + I = 820\text{ A}$ check!

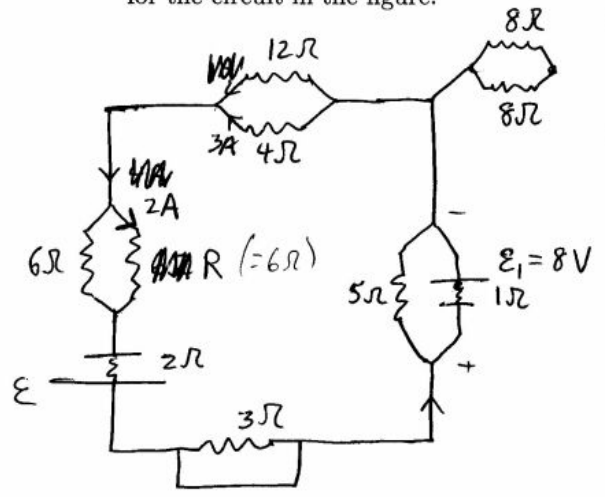7. (15 pts) Find the unknown currents, the unknown resistance, and the unknown emf for the circuit in the figure.



① $I_{12} (12) = 3(4) = 12 \Rightarrow I_{12} = 1\text{ A}$

② Thus $I = 4\text{ A}$

③ $(I - 2\text{ A}) = 2\text{ A}$, so $I = 4\text{ A}$. 2 A through $6\ \Omega$ & R , in parallel, so $R = 6\ \Omega$

④ $I_2 = 4\text{ A}$

⑤ $I_3 = 0$ (goes through wire)

⑥ $I_8 = 0$

⑦ As calculation on left shows, $\Delta V_5 = 10$, so $I_5 = \frac{\Delta V_5}{5} = \frac{10}{5} = 2\text{ A}$, and thus $I_1 = 2\text{ A}$.

⑧ Voltage drops going around circuit are $5 \times 2 + 3 \times 4 + 6 \times 2 + 4 \times 2$ or $10 + 12 + 12 + 8 = 42$, so \mathcal{E} must give rise of 42 V . $\mathcal{E} = 42\text{ V}$

$4 = I_5 + I_1$

~~$I_5 = \frac{\Delta V}{5}$~~ $I_5 = \frac{\Delta V}{5}$

$I_1 = \frac{-8 + \Delta V}{1}$

$4 = \frac{\Delta V}{5} - 8 + \Delta V$

$12 = \frac{6}{5} \Delta V$

$\Delta V = 10\text{ V}$

$10 + 12 + 12 + 8 = \mathcal{E}$
 $\mathcal{E} = 42\text{ V}$