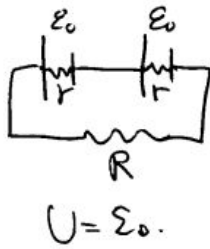


key yellow

8. (10 pts) A flashlight bulb is powered by two 1.4 V batteries in series, each with internal resistance 0.15 Ω. The batteries each lose chemical energy at the rate of 5.6 W. Determine the resistance of the lightbulb.




$$2 \cdot P = I^2(R + 2r) = \frac{(2U)^2}{R + 2r} = 5.6 \text{ W} \times 2$$


$$\therefore R = \frac{(2U)^2}{2P} - 2r = 11.2 \Omega - 0.3 \Omega = 10.9 \Omega$$

9. The capacitor is uncharged initially. The switch is then closed at  $t = 0$ . Let  $\mathcal{E} = 12 \text{ V}$ ,  $r = 4 \Omega$ ,  $R_1 = 12 \Omega$ ,  $R_2 = 6 \Omega$ ,  $C_1 = 8 \mu\text{F}$ .

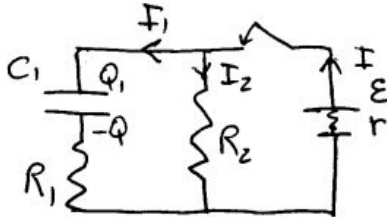- a. (10 pts) Find  $I$ ,  $Q_1$ ,  $I_1$ , and  $I_2$  just after the switch is closed. Explain.



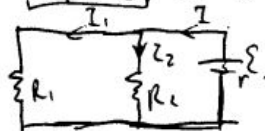①  $Q_1 = 0$  at  $t = 0$ . so circuit like




$$\therefore I = \frac{\mathcal{E}}{r + (R_1 // R_2)} = \frac{12 \text{ A}}{4 + 4} = 1.5 \text{ A}$$

$$I_1 + I_2 = I$$

$$I_1 / I_2 = R_2 / R_1 = 0.5 \Rightarrow I_1 = 0.5 \text{ A}, I_2 = 1 \text{ A}$$

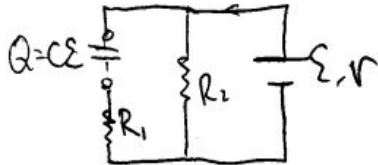- b. (10 pts) Find  $I$ ,  $Q_1$ ,  $I_1$ , and  $I_2$  a long time after the switch is closed. Explain.




$$I = I_2 = \frac{\mathcal{E}}{r + R_2} = \frac{12 \text{ V}}{(4 + 6) \Omega} = 1.2 \text{ A}$$

$$I_1 = 0$$

$$Q = C\mathcal{E} = 8 \mu\text{F} \cdot 12 \text{ V} = 96 \mu\text{C}$$

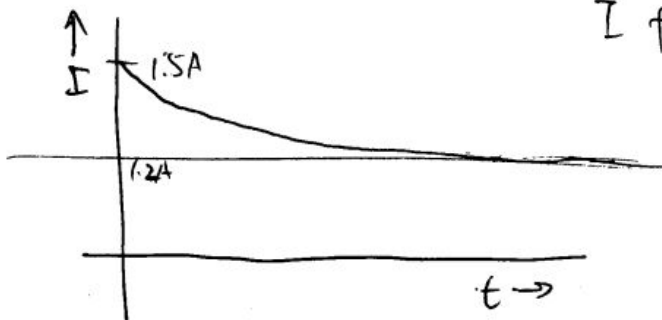- c. (5 pts) Sketch  $I$  as a function of time.



$I$  falls from 1.5 A to 1.2 A.