

Pink

Kyongwon Kim

3. (12 pts) A spherical satellite is given a charge of  $-6.5 \mu\text{C}$ , which lowers its voltage by 130 V relative to a space station that is 15 km away. Determine the capacitance and radius of the satellite. Estimate how much charge on the space station would return the satellite to its initial voltage.

$$\Delta V = \frac{k\Delta q}{r} = \frac{\Delta q}{C} \quad \text{Thus} \quad C = \frac{\Delta q}{\Delta V} = \frac{-6.5 \mu\text{C}}{-130\text{V}} = 0.05 \mu\text{F}$$


$$\text{Also, } r = \frac{k\Delta q}{\Delta V} = kC = 449.38 \text{ m}$$

$$\text{Now want } \Delta V' = \frac{kq'_{ss}}{R} = 130\text{V}$$

$$\text{So } q'_{ss} = \frac{R}{k}(130\text{V}) = 2.167 \times 10^{-4} \text{ C} = 216.7 \mu\text{C}$$


4. A voltaic cell has internal resistance  $r = 0.3 \Omega$  and open circuit voltages across the left and right electrodes of 0.4 V and 1.6 V, for a net emf of  $\mathcal{E} = 1.2 \text{ V}$ . It is in series with a resistor  $R = 0.7 \Omega$ . Let  $V_d = 0.4 \text{ V}$ . The connecting wires have zero resistance.

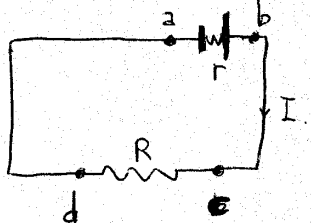a. (12 pts) Find the current, the voltage drops across the resistances, and sketch the voltage around the circuit. (Hint: start from point d.)



$$I = \frac{\mathcal{E}}{r+R} = \frac{1.2}{0.3+0.7} = 1.2 \text{ A}$$
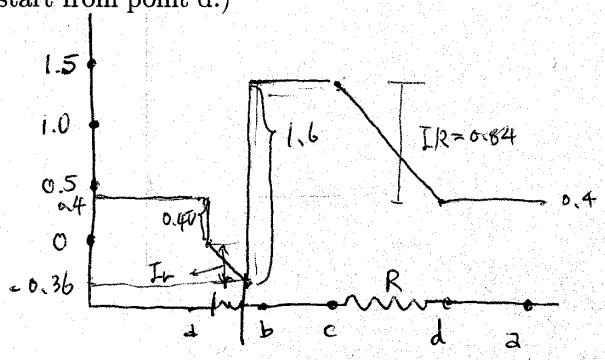
$$I_r = 0.36 \text{ V}, \quad IR = 0.84 \text{ V}$$




b. (6 pts) The cell discharges in 42 minutes; find its initial "charge" and energy.

$$Q = IT = (1.2 \text{ A}) \cdot (42 \times 60 \text{ s}) = 3024 \text{ C}$$

$$E = Q\mathcal{E} = 3629 \text{ J}$$

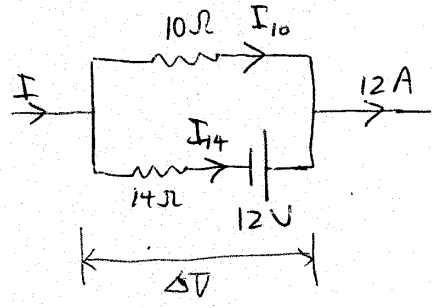5. (10 pts) Find the unknown currents for the circuit in the figure.



$$I = 12 \text{ A}$$

$$I_{10} = \frac{\Delta V}{10}, \quad I_{14} = \frac{\Delta V + 12}{14}$$

$$I = I_{10} + I_{14}$$

$$\frac{\Delta V}{10} + \frac{12}{14} + \frac{\Delta V}{14} = 12, \quad \Delta V \left( \frac{1}{10} + \frac{1}{14} \right) = 12 - \frac{12}{14} = 12 \cdot \frac{13}{14}$$

$$\Delta V = 12 \cdot \frac{13}{14} \cdot \frac{10 \cdot 14}{10+14} = \frac{12}{24} \cdot 13 \cdot 10 = 65 \text{ V}$$

$$I_{10} = \frac{65}{10} = 6.5 \text{ A}, \quad I_{14} = \frac{77}{14} = 5.5 \text{ A}$$

$$I_{10} + I_{14} = 12 \text{ A} = I \quad \checkmark$$