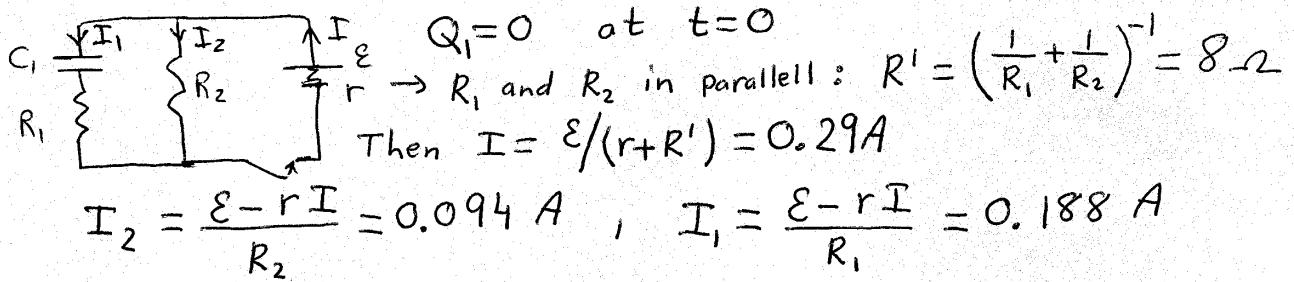


Pink

8. The capacitor is uncharged initially. The switch is then closed at $t = 0$. Let $\mathcal{E} = 4 \text{ V}$, $r = 6 \Omega$, $R_1 = 12 \Omega$, $R_2 = 24 \Omega$, $C_1 = 6 \mu\text{F}$.

a. (10 pts) Find I , Q_1 , I_1 , and I_2 just after the switch is closed. Explain.




b. (10 pts) Find I , Q_1 , I_1 , and I_2 a long time after the switch is closed. Explain.

$$I_1 \rightarrow 0 \text{ as } t \rightarrow \infty$$

$$I = I_2 = \frac{\mathcal{E}}{r + R_2} = 0.133 \text{ A}$$

$$Q_1 = C_1 \Delta V = C_1 I_2 R_2 = (6 \mu\text{F})(0.133 \text{ A})(24 \Omega) = 19.2 \mu\text{C}$$

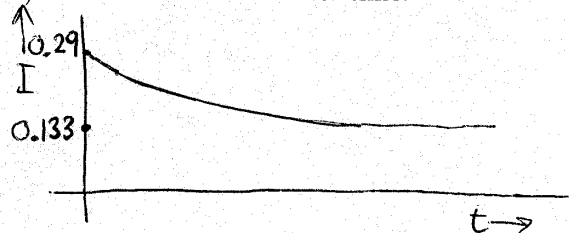c. (5 pts) Sketch I as a function of time.



9. (15 pts) A 15 cm long rod with 4 mm-by-4 mm cross-section carries 1.1 A when a voltage difference of 0.44 V is placed across its ends. Find the resistivity. Find the electric field within the rod. Estimate the drift velocity of the charge-carriers, taken to be of density $n = 2.8 \times 10^{28}/\text{m}^3$.

$$R = \frac{\Delta V}{I} = \frac{0.44}{1.1} = 0.4 \Omega$$

Resistivity: $\rho = \frac{RA}{L} = \frac{(0.4 \Omega)(4 \times 10^{-3})^2}{0.15 \text{ m}} = 4.27 \times 10^{-5} \Omega\text{m}$

Electric field: $E = \frac{\Delta V}{L} = \frac{0.44 \text{ V}}{0.15 \text{ m}} = 2.93 \text{ V/m}$

Drift velocity: $v_d = I/enA = (\Delta V/R)/enA$

$$= 1.5 \times 10^{-5} \text{ m/s}$$