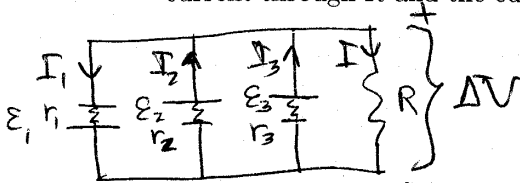


Yellow

6. (20 pts) For the circuit below, take $\mathcal{E}_1 = 12 \text{ V}$, $\mathcal{E}_2 = 20 \text{ V}$, $\mathcal{E}_3 = 16 \text{ V}$, $r_1 = 0.02 \Omega$, $r_2 = 0.01 \Omega$, $r_3 = 0.02 \Omega$, $R = 0.04 \Omega$. (1) Indicate your definitions of the directions of positive currents and of the positive side of the voltage ΔV across R . (2) Analyze the circuit using Kirchhoff's rules. (3) Solve for the voltage across R . (4) Find the current through R and the currents provided by each of the batteries.



$$I_2 + I_3 = I_1 + I$$

$$\frac{\mathcal{E}_2 - \Delta V}{r_2} + \frac{\mathcal{E}_3 - \Delta V}{r_3} = \frac{\Delta V}{R} + \frac{\mathcal{E}_1 + \Delta V}{r_1}$$

$$\frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} - \frac{\mathcal{E}_1}{r_1} = \Delta V \left(\frac{1}{R} + \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)$$

$$2000 + 800 - 600 = \Delta V (25 + 50 + 100 + 50)$$

$$\Delta V = \frac{2200}{225} = 9.78 \text{ V}$$

$$I = \frac{\Delta V}{R} = 244.4$$

$$I_1 = \frac{\mathcal{E}_1 + \Delta V}{r_1} = 1088.9$$

$$I_2 = \frac{\mathcal{E}_2 - \Delta V}{r_2} = 1022.2$$

$$I_3 = \frac{\mathcal{E}_3 - \Delta V}{r_3} = 311.1$$

} sums to 1333.3

} sums to 1333.3

7. (15 pts) You are given 60 identical voltaic cells with 1.2 V emf and 0.25 ohm internal resistance. Determine the maximum current that can be provided when these are connected so that they constitute an 18 V battery. Determine the effective internal resistance of this battery.

$$\frac{18 \text{ V}}{1.2} = 15, \text{ so use 15 cells in } \text{parallel} \text{ series}$$

Then use 4 sets of these in ~~series~~ parallel.

The maximum current of one cell is $\frac{1.2}{0.25} = 4.8 \text{ A}$,
and this is the current of the 15 cells in series.

So together, with 4 sets of 15 in parallel, $I_{\text{max}} = 4(4.8) = 19.2 \text{ A}$.

With ~~EMF~~ $\mathcal{E} = 18 \text{ V}$ and $I_{\text{max}} = \frac{\mathcal{E}}{r_{\text{eff}}}$, we have ~~EMF~~ $r_{\text{eff}} = \frac{\mathcal{E}}{I_{\text{max}}} = 0.9375 \Omega$.

3 Or: 15 of (0.25 Ω) in series is 3.75 Ω ,
and 4 of (3.75 Ω) in parallel is 0.9375.